DISTANCE ALARM

Idea: When something is in front of the sensor, it beeps. The closer it becomes to the center, the more it begins to beep.

Block Diagram

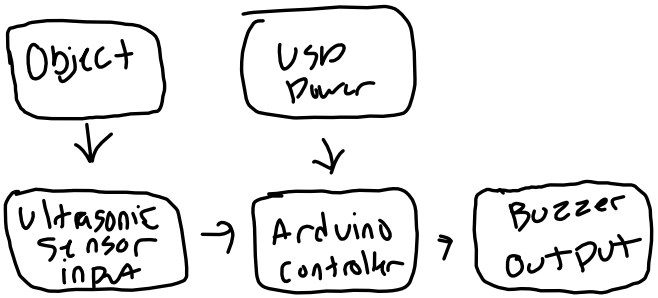

Circuit

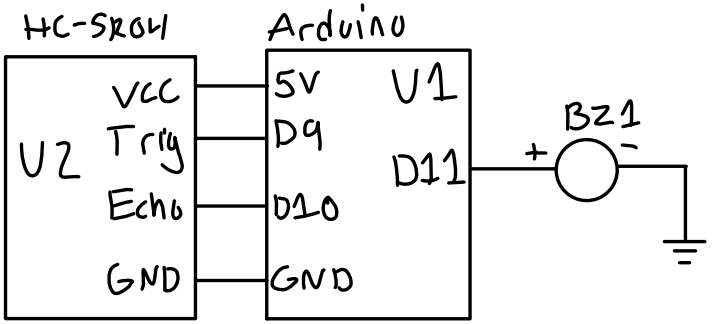

BOM

1x Arduino UNO (U1)
1x HC-SR04 Ultrasonic sensor (U2)
1x Active Buzzer (BZ1)